



CHAPTER 4 – COMBINATIONAL LOGIC




Combinational Circuits

- Two classes of logic circuits:
 - Combinational Circuits
 - Sequential Circuits
- A **Combinational circuit** consists of logic gates
 - Output depends only on input
- A **Sequential circuit** consists of logic gates and memory
 - Output depends on current inputs and previous ones (stored in memory)
 - Memory defines the state of the circuit.

Combinational Circuits

 - Output is function of input only i.e. no feedback



When **input** changes, **output** may change (after a delay)


Classification of Combinational Logic

- Arithmetic & logical functions (adder, subtractor, comparator)
- Data transmission (decoder, encoder, multiplexer, demultiplexer)
- Code converters (BCD, grey code, 7-segment)

Combinational Circuits

- Analysis

 - Given a circuit, find out its *function*
- Function may be expressed as:
 - Boolean function
 - Truth table




- Design

- Given a desired function, determine its *circuit*
- Function may be expressed as:
 - Boolean function
 - Truth table




Analysis Procedure

- Boolean Expression Approach

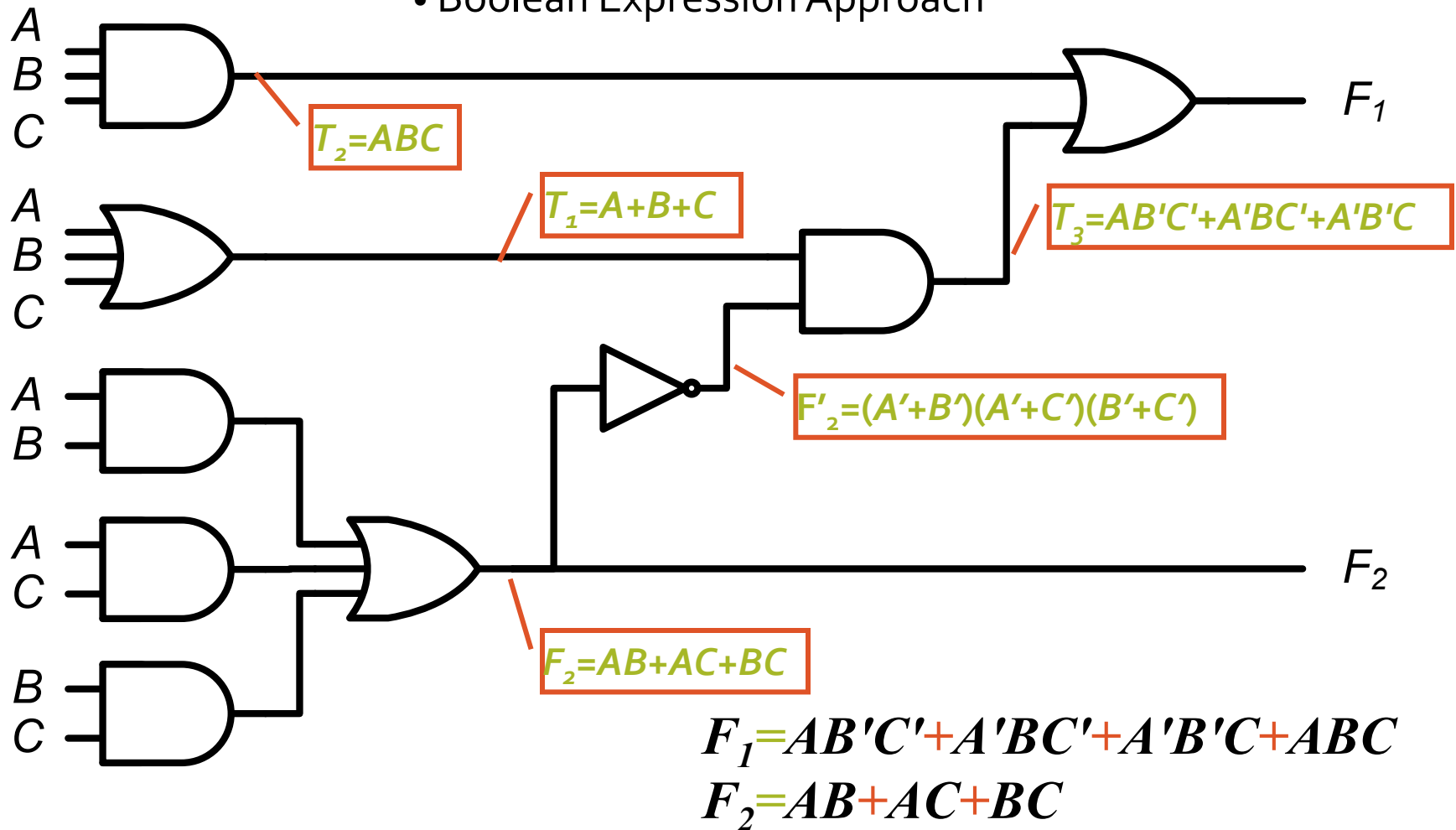


Analysis Procedure

- Truth Table Approach

 [illegible]

Analysis Procedure

- Truth Table Approach

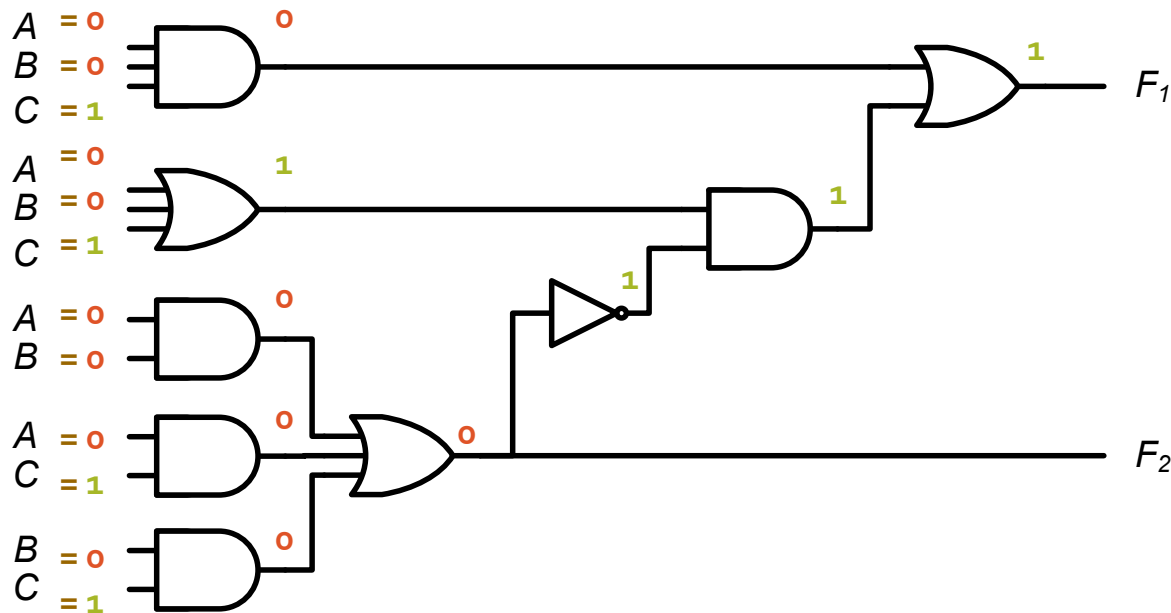


A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0

$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$

Analysis Procedure

- Truth Table Approach

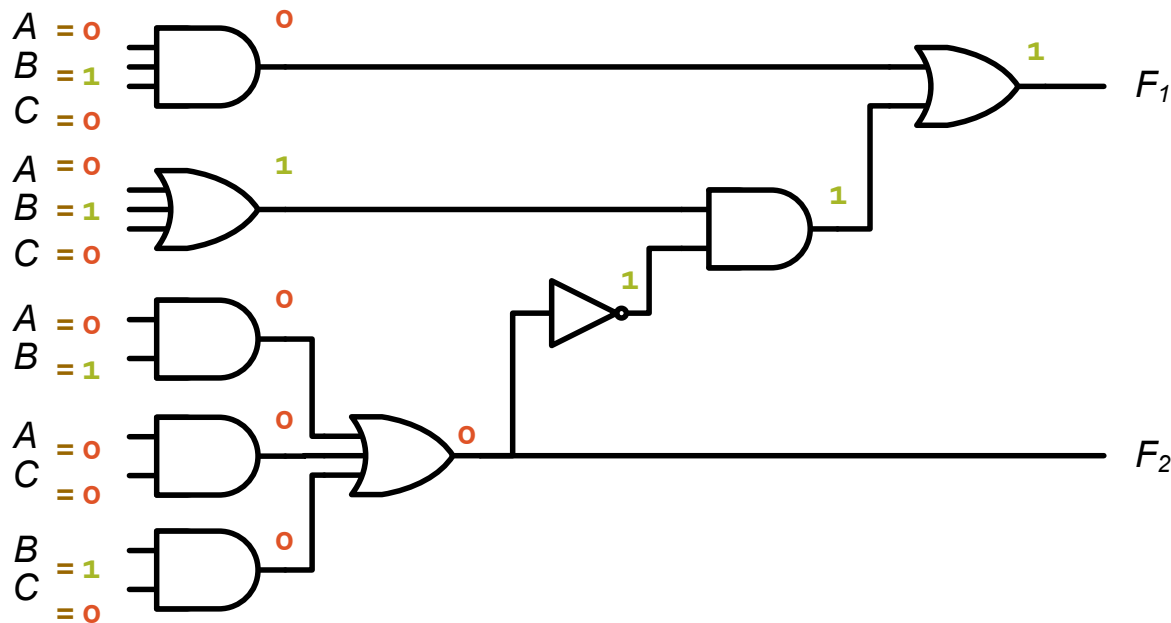


A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0

$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$

Analysis Procedure

- Truth Table Approach

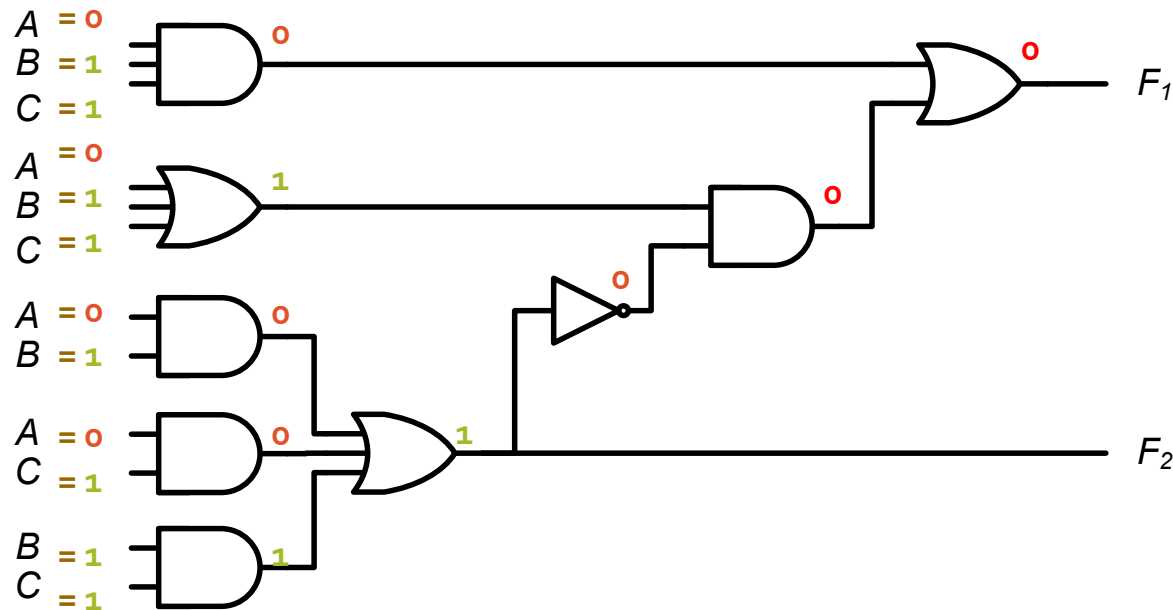


A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1

$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$

Analysis Procedure

- Truth Table Approach

 


A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0

$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$

Analysis Procedure

- Truth Table Approach

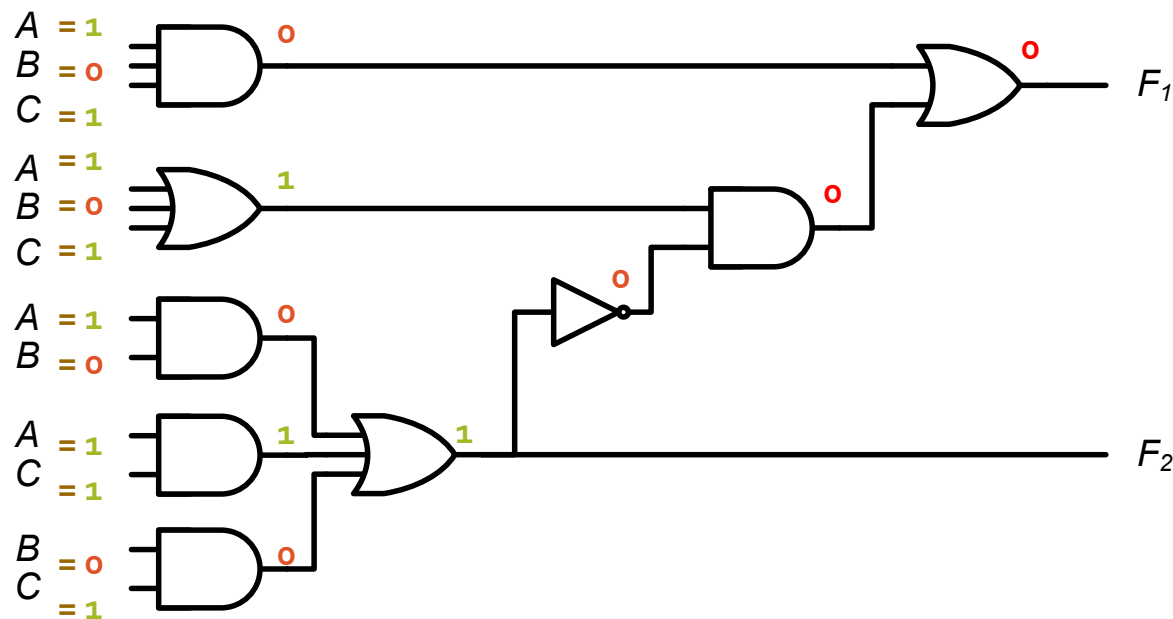


A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1

$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$

Analysis Procedure

- Truth Table Approach

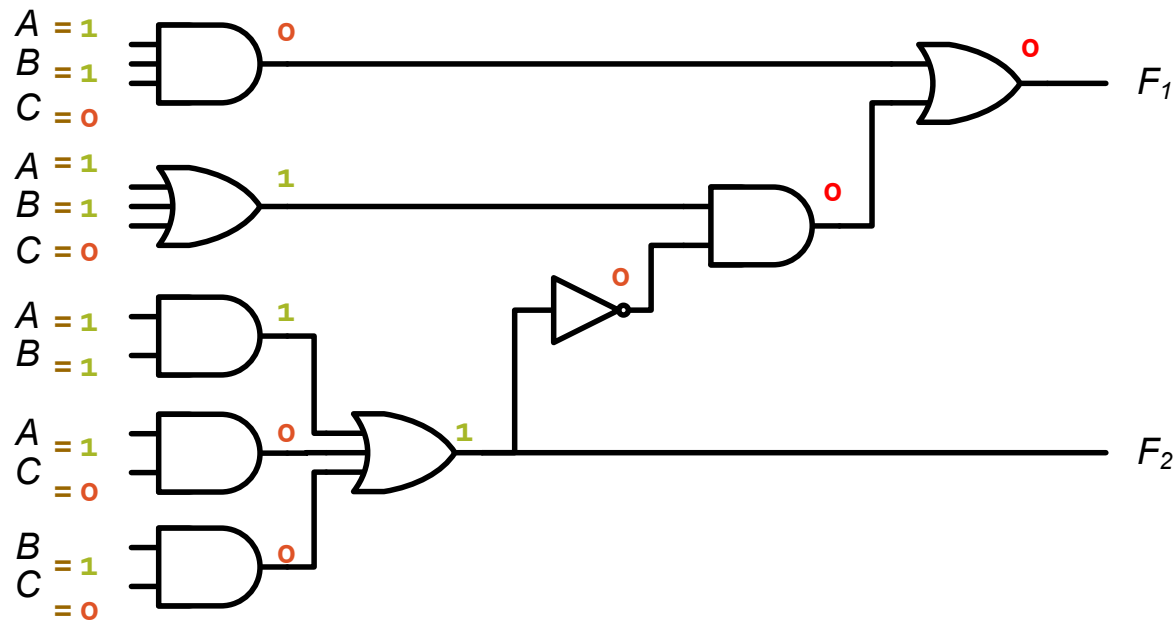


A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1

$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$

Analysis Procedure

- Truth Table Approach

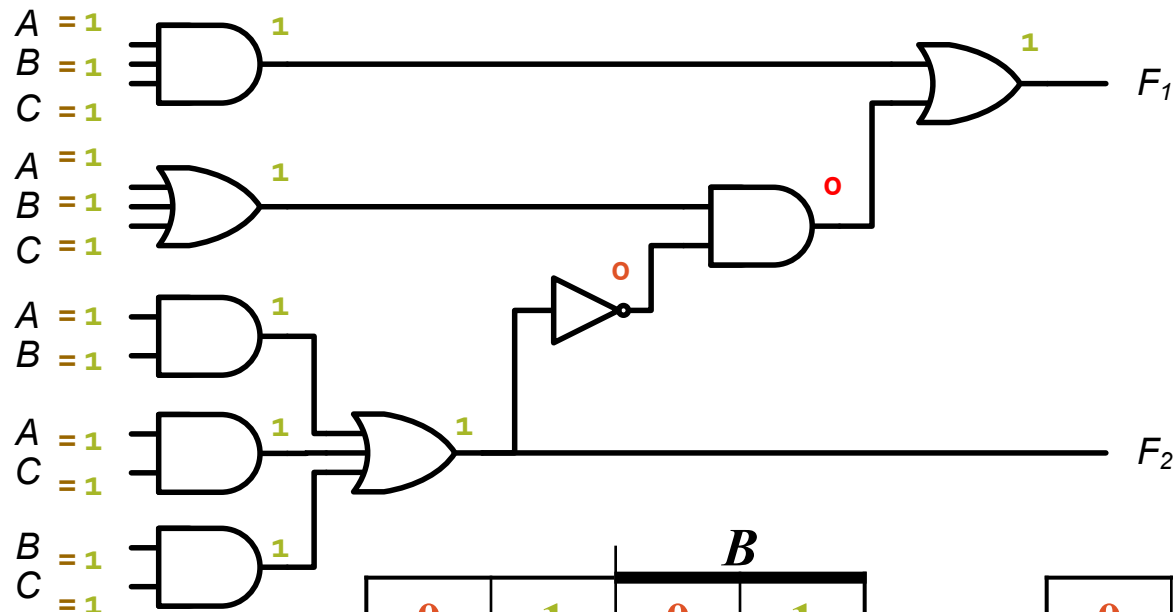

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

		B	
		0	1
A		1	0
	C	0	1

		B	
		0	1
A		0	1
	C	1	1

$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$


$$F_2 = AB + AC + BC$$

Design Procedure

- Given a problem statement:
 - Determine the number of *inputs* and *outputs*
 - Derive the truth table
 - Simplify the Boolean expression for each output
 - Produce the required circuit

 Example:


Design a circuit to convert a “BCD” code to “Excess 3” code




Design Procedure

- BCD-to-Excess 3 Converter


<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

 


$$w = A + BC + BD$$

 

$$x = B'C + B'D + BC'D'$$

 

$$y = C'D' + CD$$

 


$$z = D'$$

Design Procedure

- BCD-to-Excess 3 Converter

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

 

$$w = A + B(C+D)$$


$$x = B'(C+D) + B(C+D)'$$

$$y = (C+D)' + CD$$

$$z = D'$$




Seven-Segment converter

 - Seven-Segment Display
- A seven-segment display is digital readout found in electronic devices like clocks, TVs, etc.
 - Made of seven light-emitting diodes (LED) segments; each segment is controlled separately.



Seven-Segment converter

<i>w x y z</i>	<i>a b c d e f g</i>
0 0 0 0	1 1 1 1 1 1 0
0 0 0 1	0 1 1 0 0 0 0
0 0 1 0	1 1 0 1 1 0 1
0 0 1 1	1 1 1 1 0 0 1
0 1 0 0	0 1 1 0 0 1 1
0 1 0 1	1 0 1 1 0 1 1
0 1 1 0	1 0 1 1 1 1 1
0 1 1 1	1 1 1 0 0 0 0
1 0 0 0	1 1 1 1 1 1 1
1 0 0 1	1 1 1 1 0 1 1
1 0 1 0	x x x x x x x
1 0 1 1	x x x x x x x
1 1 0 0	x x x x x x x
1 1 0 1	x x x x x x x
1 1 1 0	x x x x x x x
1 1 1 1	x x x x x x x

   


$b = \dots$
 $c = \dots$
 $d = \dots$



Binary Adder

- Half Adder
 - Adds 1-bit plus 1-bit
 - Produces Sum and Carry

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 
  
$$\begin{array}{r} x \\ + y \\ \hline C \quad S \end{array}$$



Binary Adder

- Full Adder
 - Adds 1-bit plus 1-bit plus 1-bit
 - Produces Sum and Carry



x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

	y			
	0	1	0	1
x	1	0	1	0
	z			

$$S = xy'z' + x'y'z + x'yz + xyz = x \oplus y \oplus z$$

	y			
	0	0	1	0
x	0	1	1	1
	z			

$$C = xy + xz + yz$$



$$\begin{array}{r}
 x \\
 + y \\
 + z \\
 \hline
 C \quad S
 \end{array}$$

Binary Adder

- Full Adder

$$S = xy'z' + x'yz' + x'y'z + xyz = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

  


Full Adder = 2 Half Adders


Manipulating the Equations:

$$S = (X \oplus Y) \oplus Z$$
 
$$C = XY + XZ + YZ = XY + Z(X \oplus Y)$$



Binary Adder

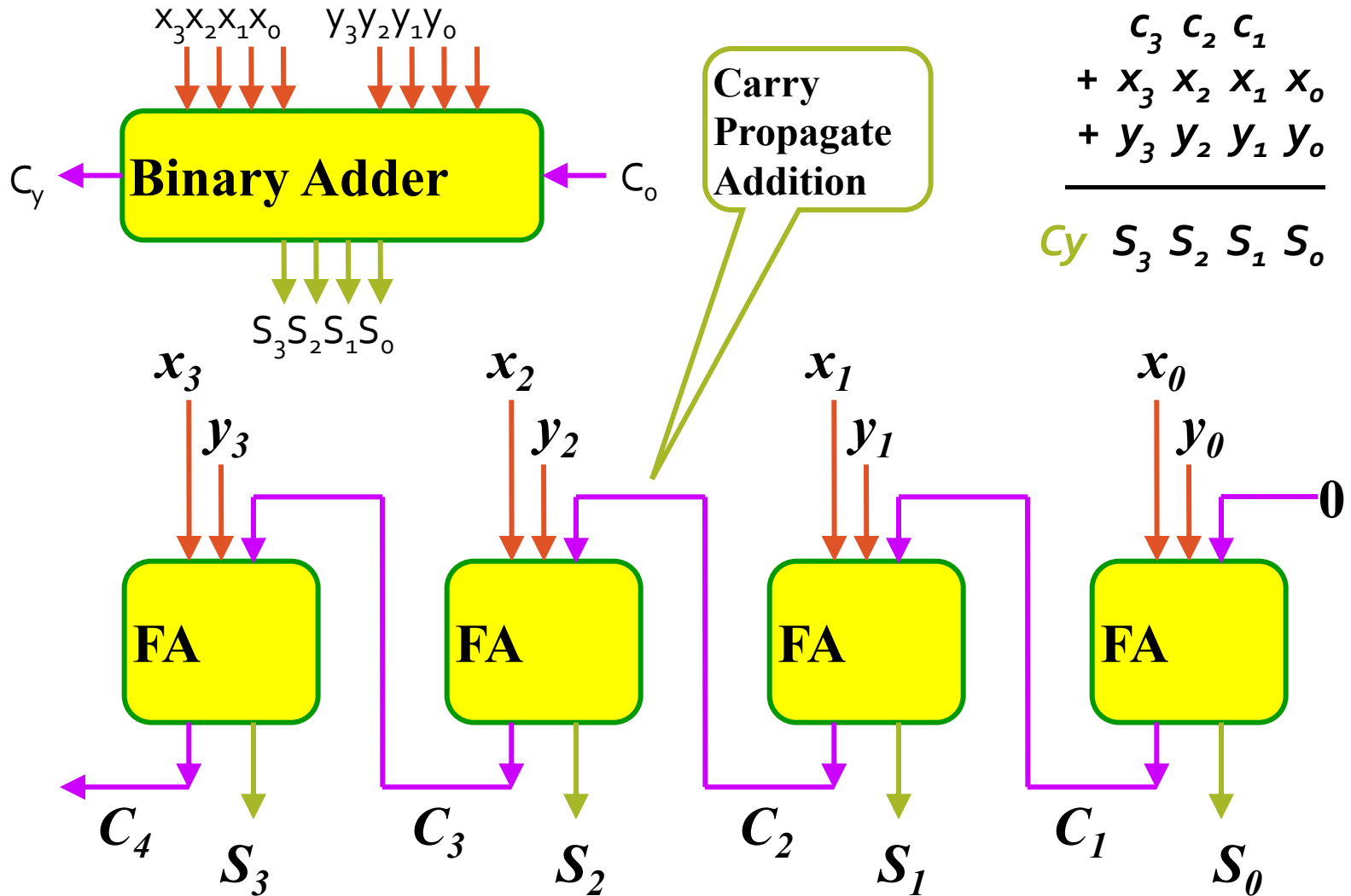

Bigger Adders

- How to build an adder for n-bit numbers?
 - Example: 4-Bit Adder
 - Inputs ?
 - Outputs ?
 - What is the size of the truth table?
 - How many functions to optimize?

Bigger Adders

- How to build an adder for n-bit numbers?
 - Example: 4-Bit Adder
 - Inputs ? 9 inputs
 - Outputs ? 5 outputs
 - What is the size of the truth table? 512 rows!
 - How many functions to optimize? 5 functions

Binary Adder

$$\begin{array}{r} 1\ 0\ 0\ 0 \\ 0\ 1\ 0\ 1 \\ +\ 0\ 1\ 1\ 0 \\ \hline 1\ 0\ 1\ 1 \end{array}$$

← Carry in

- To add n-bit numbers:
- Use n Full-Adders in Cascade.
- The carries propagates as in addition by hand.

This adder is called *ripple carry adder*

Binary Subtractor

- Half Subtractor

A logic circuit which is used for subtracting one single bit binary number from another single bit binary number is called half subtractor.

Binary Subtractor

- Half Subtractor

S.No	INPUT		OUTPUT	
	A	B	DIFF	BORR
1.	0	0	0	0
2.	0	1	1	1
3.	1	0	1	0
4.	1	1	0	0

Binary Subtractor

- Full Subtractor

The Full subtractor is a combinational circuit which is used to perform subtraction of three bits.

Binary Subtractor

- Full Subtractor

S.No	INPUT			OUTPUT	
	A	B	C	DIFF	BORR
1.	0	0	0	0	0
2.	0	0	1	1	1
3.	0	1	0	1	1
4.	0	1	1	0	1
5.	1	0	0	1	0
6.	1	0	1	0	0
7.	1	1	0	0	0
8.	1	1	1	1	1

Binary Subtractor


- Derive simplified Boolean expressions for Half Subtractor and Full Subtractor.

Subtraction (2's Complement)

- How to build a subtractor using 2's complement?

Subtraction (2's Complement)

 - How to build a subtractor using 2's complement?




$$S = A + (-B)$$

Adder/Subtractor

- How to build a circuit that performs both addition and subtraction?

Adder/Subtractor

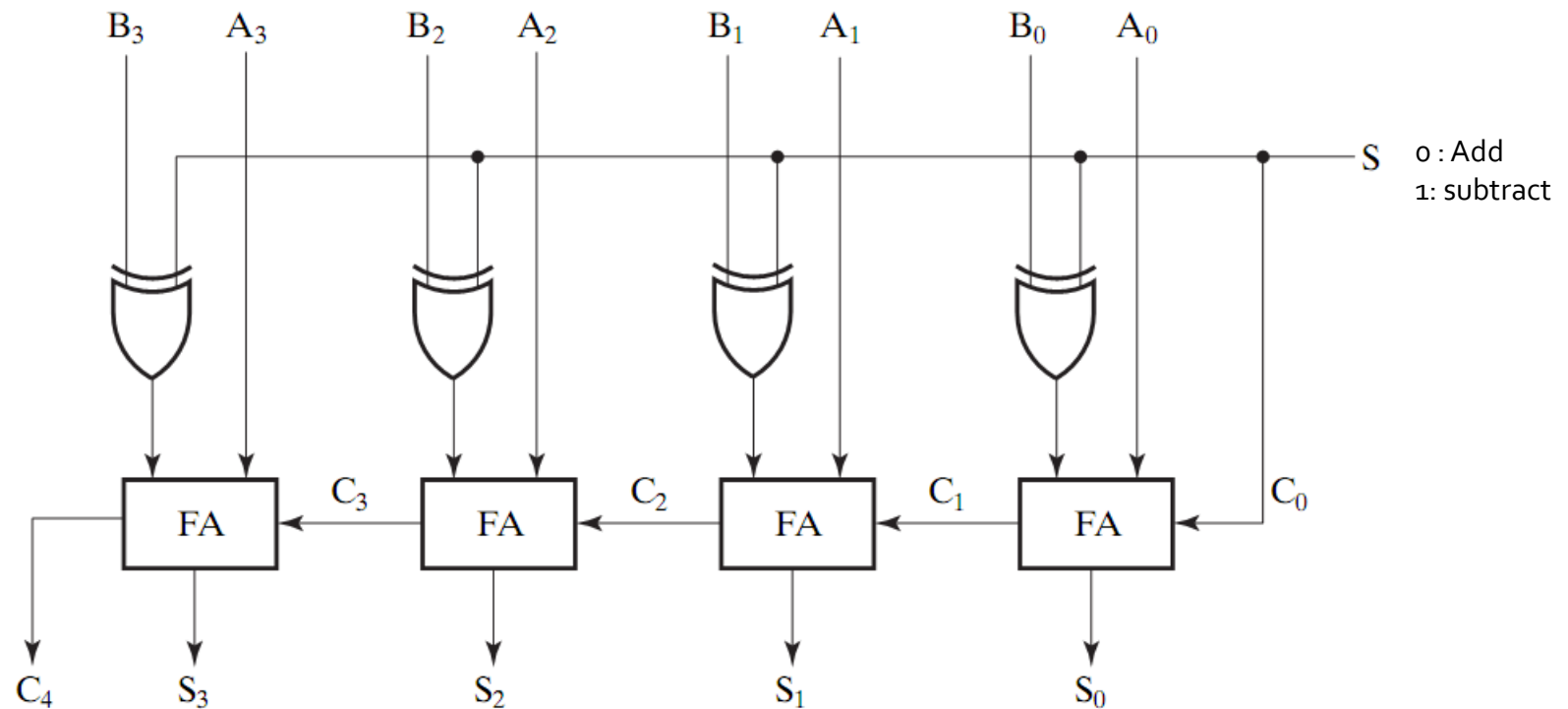

Using full adders and XOR we can build an Adder/Subtractor!